
 


Emitter-Coupled Logic (ECL)

 


The ECL Advantage




- *All of the BJT-based logic gates discussed so far use the transistors as saturated switches.*
- *In addition, operation of the RTL, DTL, and TTL gates involves relatively large voltage swings on the p-n junctions.*
- *ECL gates are inherently FASTER than the other BJT-based logic gates because the transistors stay forward active and the voltage swings are small.*
- *The fastest commercially-available logic gates are made with ECL at the present time: sub-nanosecond propagation delays make possible off-chip data rates approaching 1 GHz.*

Basic ECL Current Switch

 

- The ECL current switch acts like a differential amplifier with a fixed reference voltage at the base of Q_R .
- If $V_{IN} > V_{REF}$, Q_I conducts and V_{INV} goes low. Q_R cuts off, and V_{NINV} goes high.
- If $V_{IN} < V_{REF}$, Q_R conducts and V_{NINV} goes low. Q_I cuts off and V_{INV} goes high.
- The current in R_E , and hence the power dissipation, are nearly constant.

Basic ECL: Choice of V_{REF}

 

- With a high input, $V_{IN} = V_{CC}$,

$$V_E \approx$$


- Q_R can be held off as long as

$$V_{BE2} \leq$$

- V_{REF} can thus be chosen as

$$V_{REF} =$$

Basic ECL: Conduction of Q_R

 

- With a low input, and Q_I off,


$$V_E =$$

- To maintain a symmetric cut-off situation, we design so that

$$V_{BEI} = \quad V_{OL} =$$

- This may be achieved through the choice of R_C , but then Q_R is near saturation!


Improved ECL Gate

 

- Emitter followers have been added at the output.
- The fan-out is improved.
- The speed is improved.
- Q_R conducts safely in the forward active region.
- The outputs are referenced to ground for better noise immunity.

Motorola ECL I, or MECL I, was the first standard family of ECL gates and utilized the basic design shown here, with a -5.2V supply and a fixed reference voltage.

Motorola ECL I: VTC

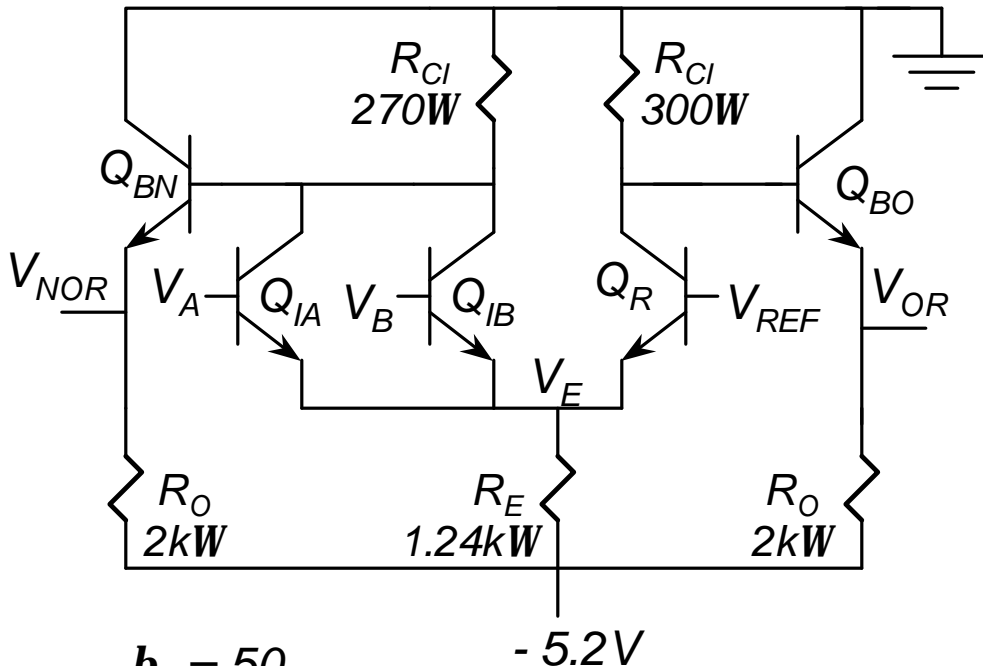

$$\begin{aligned}
 b_F &= 50 \\
 V_{BEA} &= 0.75V \\
 V_{REF} &= -1.175V
 \end{aligned}$$

Approximate analysis:

Assuming a transition width of 0.1V at the input,

$$V_{IL} =$$

$$V_{IH} =$$


If we neglect the base currents flowing through R_{CI} and R_{CR} :

$$V_{OL} =$$

$$V_{OH} =$$

$$\text{Hence } \frac{V_{OL} + V_{OH}}{2} \approx$$

Motorola ECL I: Dissipation

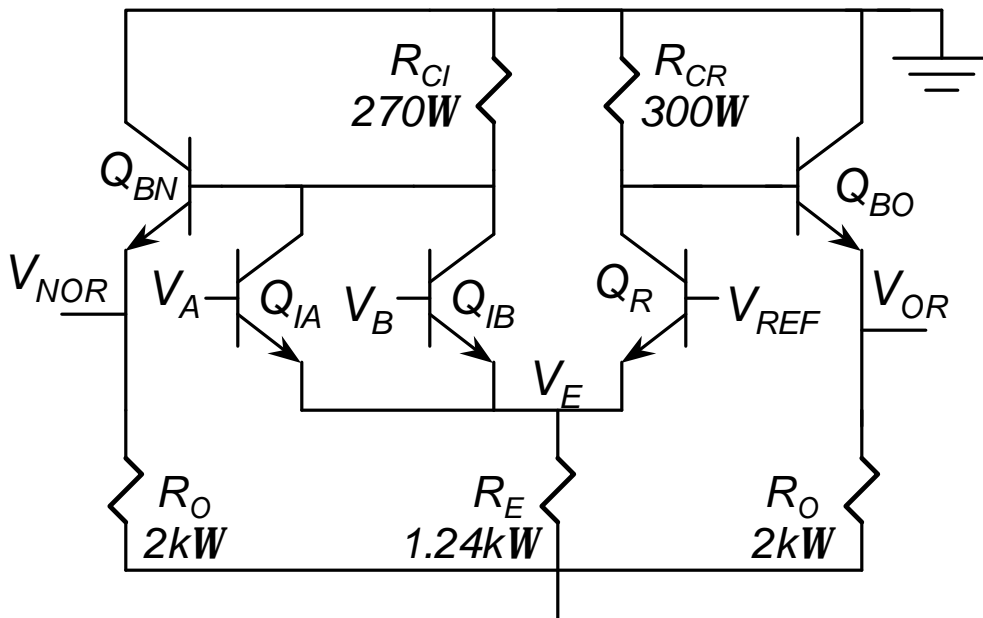

With Q_R conducting,

$$P_L =$$

With Q_{IA} or Q_{IB} conducting,

$$P_H =$$

$$b_F = 50$$

$$V_{BEA} = 0.75V$$

$$V_{REF} = -1.175V$$

NOTE: P_H and P_L are defined with respect to the noninverting output.

ECL: Temperature Effects

- *For a fixed level of current, the forward voltage across a PN junction decreases with increasing temperature*

$$\left. \frac{dV}{dT} \right|_{\text{fixed current}} =$$

Experimental values are approximately -2mV / °C

- *V_{OL} and V_{OH} therefore move toward ground as the temperature increases*
- *With a fixed V_{REF} , ECL malfunctions for $T > 60$ °C. ECL II uses a temperature-compensated bias driver.*

ECL: Temperature Effects

- *Temperature dependence of V_{OH} :*

$$\frac{dV_{OH}}{dT}$$


- *Temperature dependence of V_{OL} :*

$$V_{OL} =$$

$$\frac{dV_{OL}}{dT} =$$

- *To stay centered between V_{OH} and V_{OL} , V_{REF} should increase approximately $1.5\text{mV}/^\circ\text{C}$.*

Standard ECL Gates

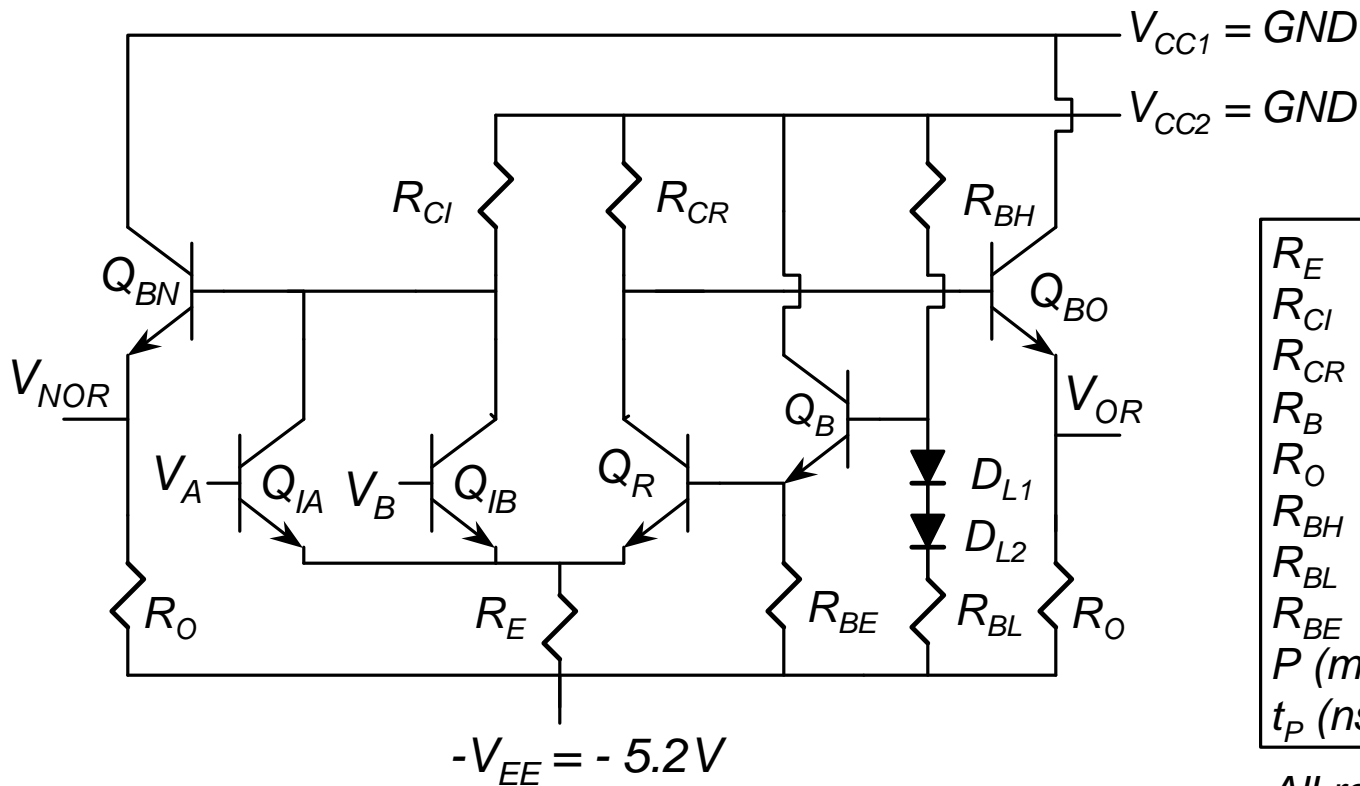


	II	10k	III
R_E	1.18	0.78	0.365
R_{CI}	0.29	0.22	0.100
R_{CR}	0.30	0.245	0.112
R_B	-	50	50
R_O	2.0	-	-
R_{BH}	0.30	0.91	0.35
R_{BL}	2.3	5.0	1.96
R_{BE}	2.0	6.1	2.0
P (mW)	20	25	60
t_p (ns)	4	2	1

All resistors are in kilohms.

The ECL II, ECL 10k, and ECL III families all use the same circuit design and voltage supplies. The differences: resistor values and transistor device designs yield differences in power / speed performance.

Standard ECL Performance

 

$$t_p \propto R_C$$

$$P \propto \frac{1}{R_C}$$

$$PDP \propto \frac{R_C}{R_C}$$

For a particular BJT design, the PDP is independent of R_C .

Switching Speed of ECL

- *For ECL, the switching speed is limited by the charging of parasitic capacitances through finite resistors, internal to the gate. External RC time constants tend to be unimportant.*

- *C_{BC} and C_P are the important capacitances.*

- *R_C is the important resistance.*


- *ECL is very fast due to:*
 - *the small logic swing*
 - *the avoidance of saturated operation in transistors*
 - *The use of a low-impedance emitter follower to drive the load.*

Switching Speed of ECL

- Consider the turn-off of Q_I in a two-input gate. At the collector of Q_I :

$$V_{CI}(t) =$$

 - Solving for $V_{CI}(t) = V_{CI}(0) / 2$, $t_P =$



<i>family</i>	R_C	C_{BC}	t_P (calc.)	t_P (meas.)
<i>ECL II</i>	295W	4 pF	4.1 ns	4.0 ns
<i>ECL 10k</i>	232W	3 pF	2.4 ns	2.0 ns
<i>ECL III</i>	106W	3 pF	1.1 ns	1.0 ns
<i>ECL 100k</i>	150W	1.5 pF	0.78 ns	0.75 ns


ECL 100k

- *Vintage 1985*
- *Oxide-isolated transistors, similar to those used in 74F TTL, reduce the parasitic capacitances and improve switching speed.*
- *A reduced supply voltage (4.5V vs 5.2V) reduces dissipation.*
- *Improved temperature compensation makes V_{OH} , V_{OL} , and V_{REF} almost independent of temperature ($< 0.1\text{mV}/^\circ\text{C}$ for all)*
- *A current source, driven by a second voltage reference, minimizes voltage supply sensitivity.*

$$\frac{\Delta V_{OL}}{\Delta V_{EE}} = -0.25 \quad (\text{ECL } 10\text{k})$$

$$\frac{\Delta V_{OL}}{\Delta V_{EE}} = -0.01 \quad (\text{ECL } 100\text{k})$$

ECL 100k

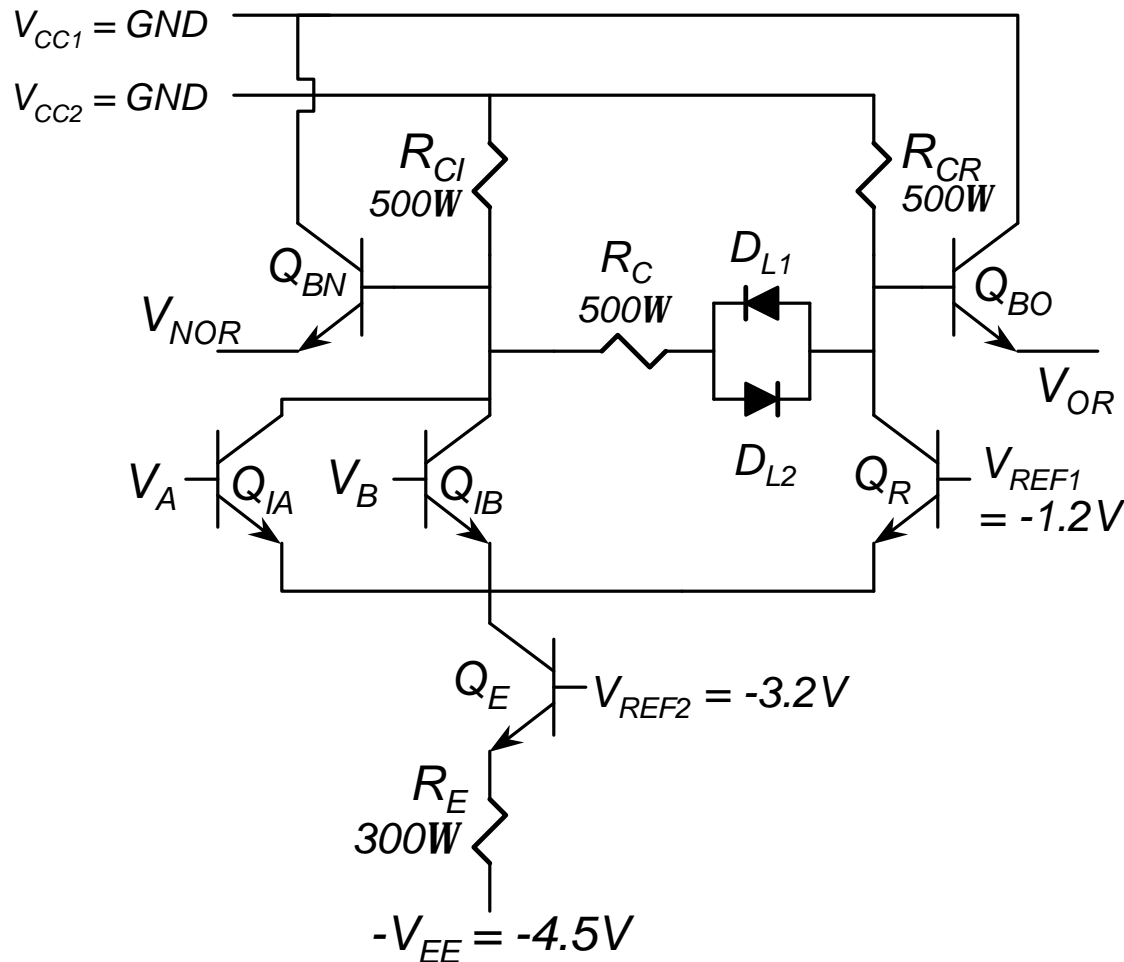

- V_{REF1} is designed to be independent of temperature and supply voltage.

- V_{REF2} is independent of temperature but varies with V_{EE} such that

$$V_{REF2} - (-V_{EE}) = \text{constant}$$

$$I_{EE} = \text{constant}$$

- D_{L1} and D_{L2} provide output voltage T compensation

ECL 100k


Consider a low output at V_{OR} , with Q_R and D_{L2} conducting:

$$I_1 =$$

$$I_2 =$$

$$I_{EE} =$$

$$V_{OL} =$$

 

ECL 100k


Consider a high output at V_{OR} , with Q_1 and D_{L1} conducting:

$$I_2 =$$


$$I_1 =$$

$$I_{EE} =$$

$$V_{OH} =$$

 

ECL 100K Bias Driver

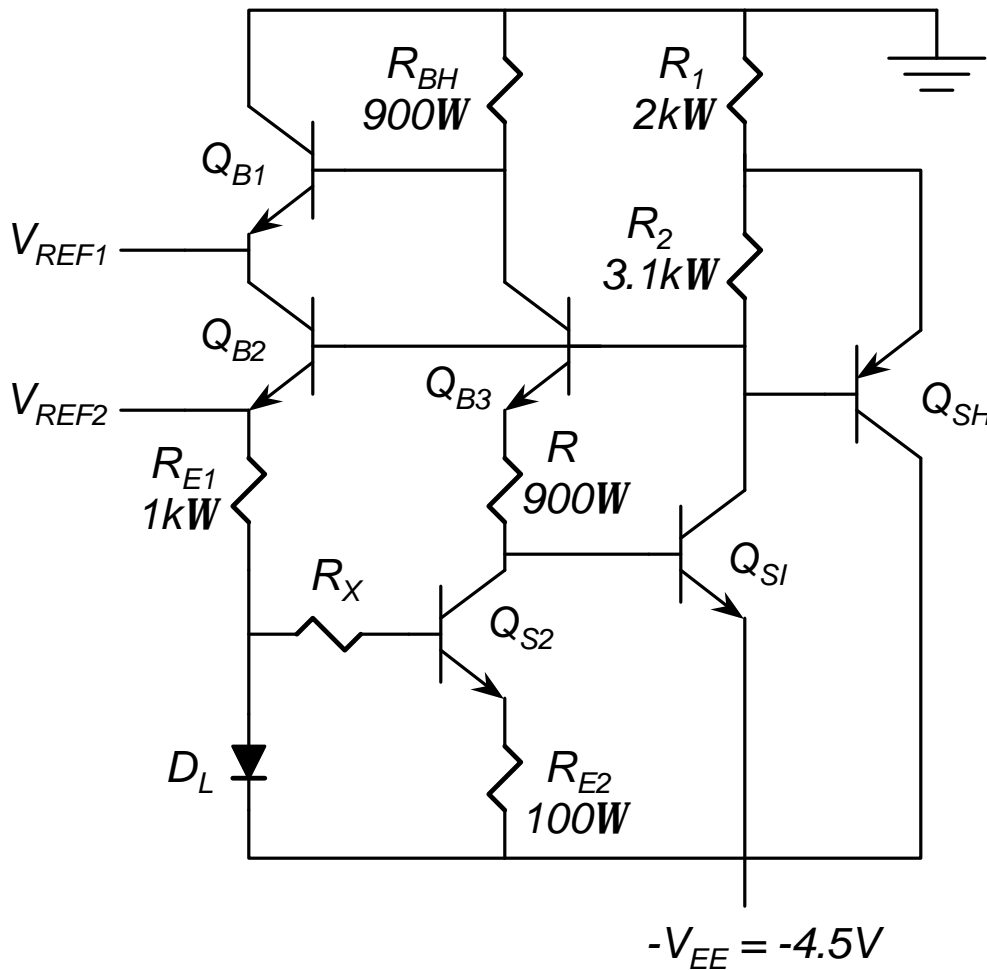

V_{REF1} is compensated for variations in T and V_{EE} :


$$V_{REF1} =$$

$$I_{CB3} \approx$$

$$V_{REF1} =$$

The circuit is designed such that I_{ES2} has a positive temperature coefficient, which cancels the negative coefficient for V_{BEA} .

ECL 100K Bias Driver

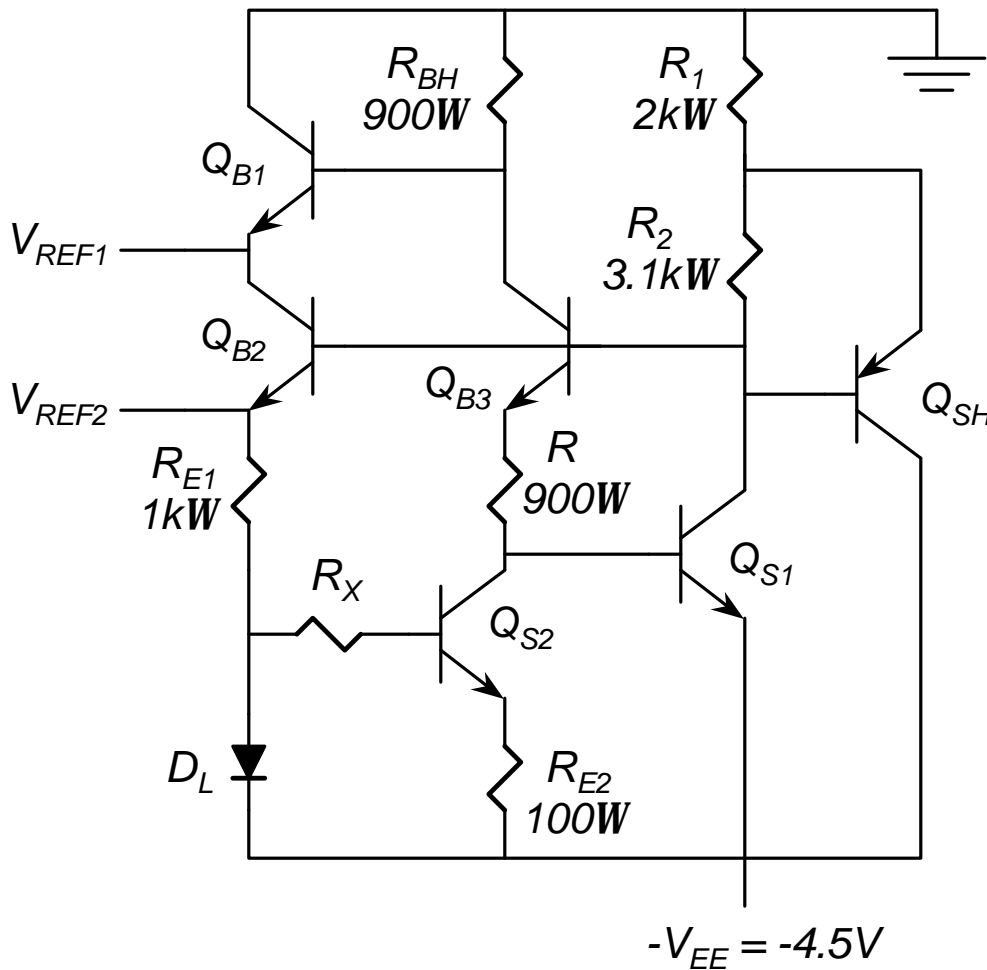

V_{REF2} is T compensated:

$$V_{REF2} =$$

$$V_{REF2} =$$

The temperature compensation is the same as for V_{REF1} . Also, V_{REF2} varies directly with $-V_{EE}$, so that $V_{REF2} - (-V_{EE})$ is fixed.

The shunt regulator Q_{SH} guarantees fixed currents in Q_{S1} , Q_{S2} , and Q_{B3} .

ECL Applications and Trends

- *Si ECL gates are important for high data rate applications, such as vector architecture supercomputers.*
- *Massively parallel processor (MPP) and Symmetric Multiprocessing (SMP) architectures will continue to bring CMOS and BiCMOS into the supercomputer arena at the expense of ECL.*
- *Nonetheless, ECL is projected to hold a significant market share among Si digital IC's until at least 2005 A.D.*
- *New materials and devices, such as GaAs/AlGaAs and Si/SiGe heterojunction bipolar transistors, may create a rebirth of ECL by boosting switching speeds to a new plateau (> 1 GHz).*