

---

# Lecture 11:

## Single-Stage BJT Amplifiers

Gu-Yeon Wei  
Division of Engineering and Applied Sciences  
Harvard University  
guyeon@eecs.harvard.edu

# Overview

---

- **Reading**
  - S&S: Chapter 4.11
- **Supplemental Reading**
- **Background**
  - Given our understanding of small-signal models and analysis, we continue our investigation of BJT circuits by looking at single-stage BJT amplifiers of various configurations. While there is a lot more detail we can discuss in terms of BJTs and their large signal behavior, we will stop with the discussion of BJT amplifiers and continue next lecture with MOSFETs which we will focus on for the rest of the semester.
  - For more information on BJT circuits, read S&S 4.12~15


# Single-Stage Amplifier Configurations

---

- There are three basic configurations for single-stage BJT amplifiers:
  - Common-Emitter
  - Common-Base
  - Common-Collector
- Let's look at these amplifier configurations and their small-signal operation

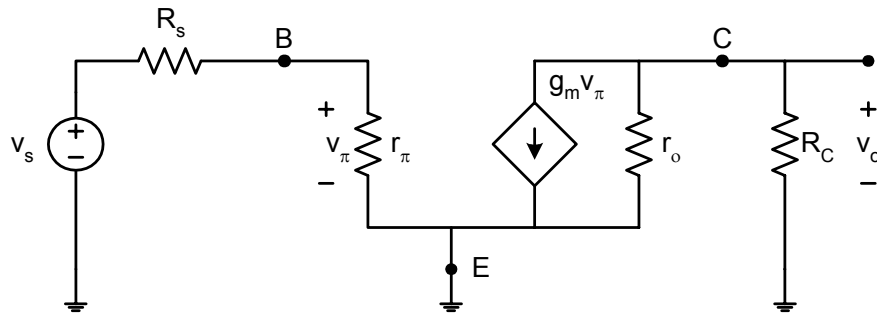
# Common-Emitter Amplifier

- First, assume  $R_e = 0$  (this is not  $r_e$ , but an explicit resistor)
- The BJT is biased with a current source (with high output impedance) and a capacitor connects the emitter to ground.
  - Cap provides an AC short at the emitter for small time-varying signals but is an open circuit for DC signals
- Can redraw the circuit with an equivalent circuit that replaces the BJT with its hybrid- $\pi$  model



$$\frac{v_\pi}{v_s} = \frac{r_\pi}{R_s + r_\pi} \quad v_o = -g_m v_\pi (R_C \parallel r_o) \quad \frac{v_o}{v_\pi} = -g_m (R_C \parallel r_o)$$
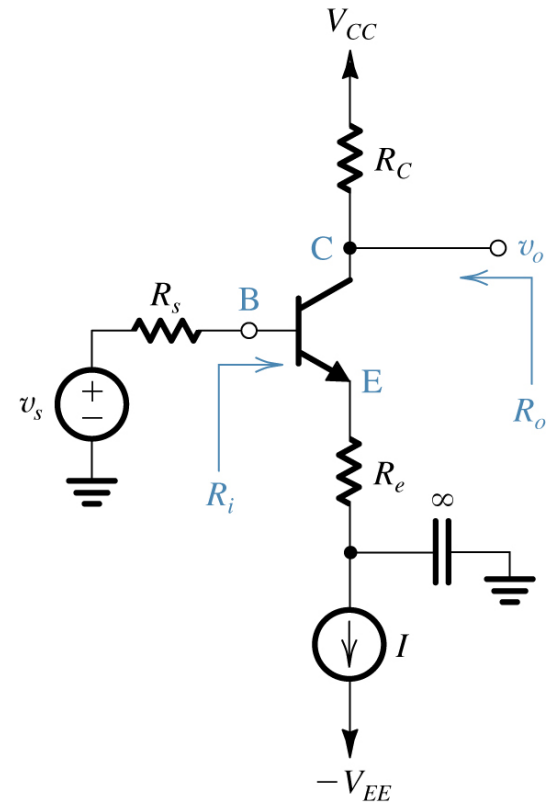
$$\frac{v_o}{v_s} = \frac{v_o}{v_\pi} \frac{v_\pi}{v_s} = -\frac{r_\pi}{R_s + r_\pi} g_m (R_C \parallel r_o) = -\frac{\beta (R_C \parallel r_o)}{R_s + r_\pi}$$



$$R_{in} = r_\pi \quad R_o = r_o \parallel R_C$$

# CE Amp with Emitter Degeneration

- Now, assume  $R_e \neq 0$ . First, find  $R_i$ ...
  - voltage applied to the base is across  $r_e$  and  $R_e$

$$v_b = i_e (r_e + R_e)$$

- base current is

$$i_b = \frac{i_e}{1 + \beta}$$


- and let's us find  $R_i$

$$R_i \equiv \frac{v_b}{i_b} = (\beta + 1)(r_e + R_e)$$

- this tells us that adding  $R_e$  increases the input resistance

$$\frac{R_i (\text{w/ } R_e)}{R_i (\text{w/o } R_e)} = 1 + \frac{R_e}{r_e} = 1 + g_m R_e$$

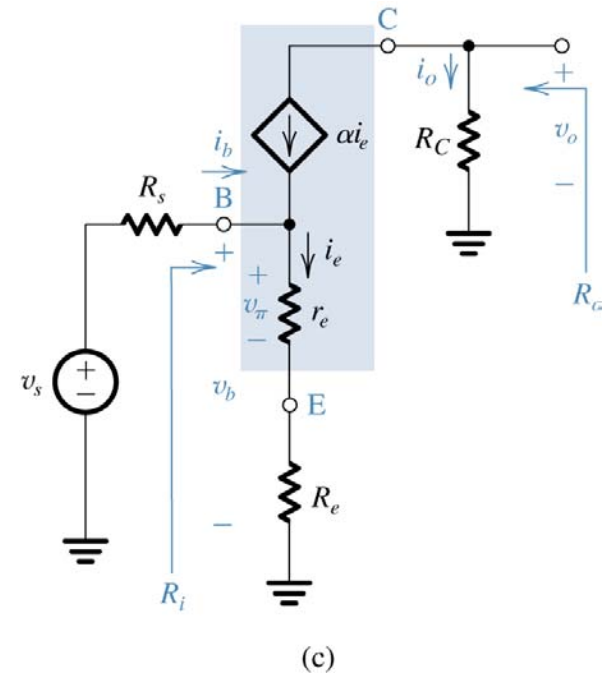- Can design the desired  $R_i$  by setting  $R_e$



- To determine the voltage gain, first find the gain from the base to the collector (ignore  $r_o$  b/c it complicates the analysis considerably)

$$v_o = -\alpha i_e R_C \quad v_b = i_e (r_e + R_e)$$

$$\frac{v_o}{v_b} = \frac{-\alpha R_C}{r_e + R_e} \cong \frac{-R_C}{r_e + R_e}$$


- **NOTE:** Voltage gain between base and collector is equal to ratio of total resistance in the collector to the total resistance in the emitter.

- To find the total gain,

$$\frac{v_o}{v_s} = \frac{v_o}{v_b} \frac{v_b}{v_s} = \frac{R_i}{R_i + R_s} \frac{-R_C}{r_e + R_e} = -\frac{\beta R_C}{R_s + (\beta + 1)(r_e + R_e)}$$



- Characteristics with  $R_e$  :

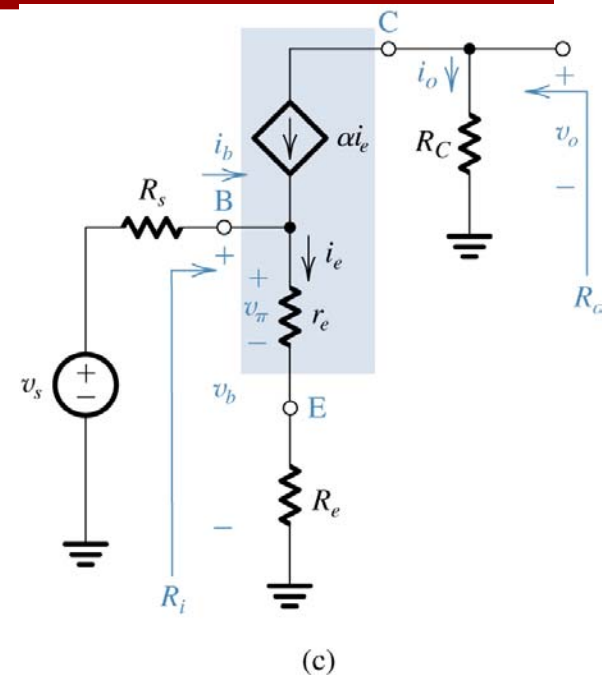- gain is less with but less dependent on  $\beta$
- input resistance is higher
- allows higher input signal voltage


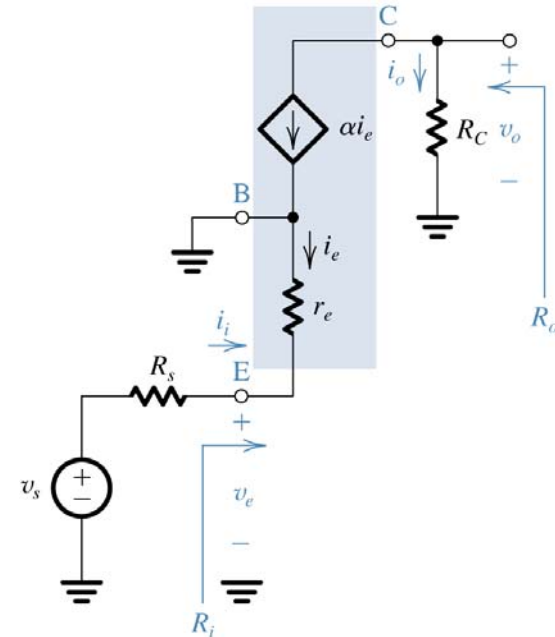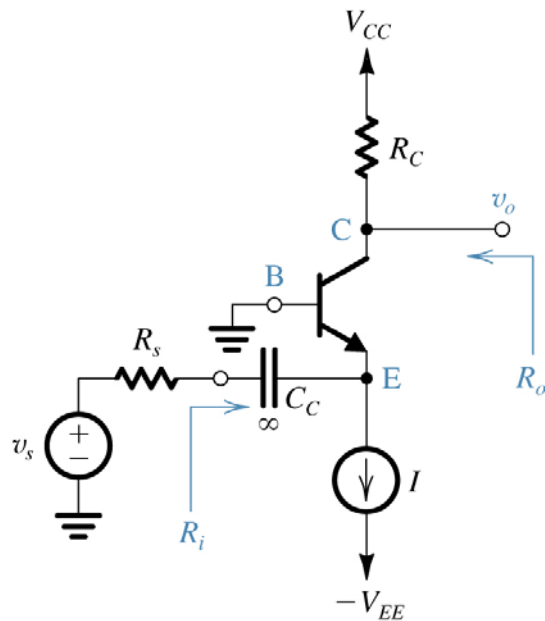
# Common-Base Amplifier

- This time, ground the base and drive the input signal into the emitter through a coupling capacitor (only passes ac signals)



- Model the small signal approximation with a T-model
  - current source is an AC open and  $C_C$  is an AC short


- First, we can see that...

$$R_i = r_e$$

- To find the gain, solve for  $v_o$

$$v_o = -\alpha i_e R_C \quad i_e = -\frac{v_s}{R_s + r_e} \quad A \equiv \frac{v_o}{v_s} = \frac{\alpha R_C}{R_s + r_e}$$


- The output impedance is just  $R_o = R_C$
- CB amp characteristics:
  - voltage gain has little dependence on  $\beta$
  - gain depends critically on  $R_s$
  - is non-inverting
  - most commonly used as a unity-gain current amplifier or current buffer and not as a voltage amplifier: accepts an input signal current with low input resistance and delivers a nearly equal current with impedance
  - most significant advantage is its excellent frequency response

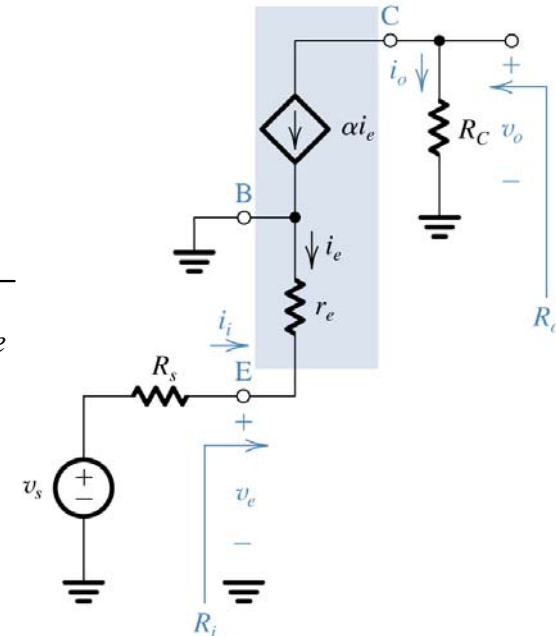


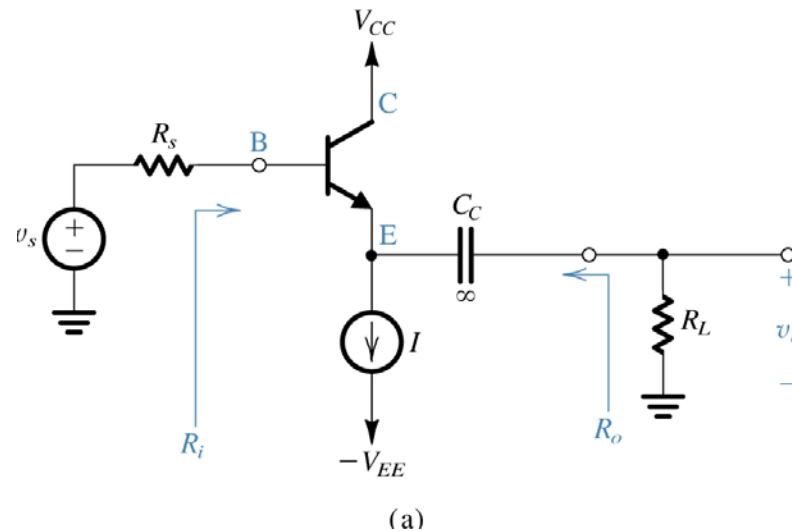
# Common-Collector Amplifier (Emitter Follower)

- The last basic configuration is to tie the collector to a fixed voltage, drive an input signal into the base and observe the output at the emitter




- Also called an emitter follower since the emitter follows the input signal
- Used for connecting a source with a large  $R_s$  to a load with low resistance

- Redraw the circuit to have  $r_o$  in parallel with  $R_L$ 
  - now, find  $R_i$   $R_i = (\beta + 1)[r_e + (r_o \parallel R_L)]$
  - when  $r_e \ll R_L \ll r_o$   $R_i \cong (\beta + 1)R_L$
  - notice the amplifier has large input resistance
- Find the gain with two voltage dividers

$$\frac{v_b}{v_s} = \frac{(\beta + 1)[r_e + (r_o \parallel R_L)]}{R_s + (\beta + 1)[r_e + (r_o \parallel R_L)]} \quad \frac{v_o}{v_b} = \frac{r_o \parallel R_L}{r_e + r_o \parallel R_L}$$


$$A_v \equiv \frac{v_o}{v_s} = \frac{(\beta + 1)(r_o \parallel R_L)}{R_s + (\beta + 1)[r_e + (r_o \parallel R_L)]} = \frac{r_o \parallel R_L}{\frac{R_s}{\beta + 1} + r_e + (r_o \parallel R_L)}$$

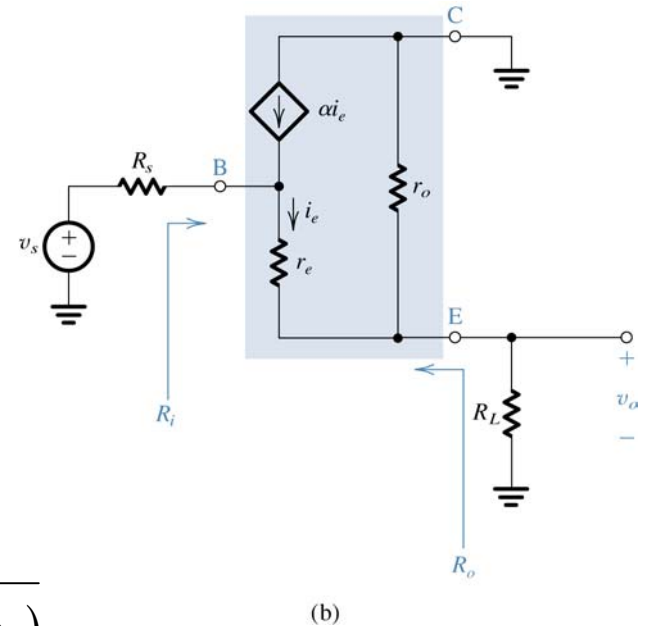- gain is less than unity, but close (to unity) since  $\beta$  is large and  $r_e$  is small


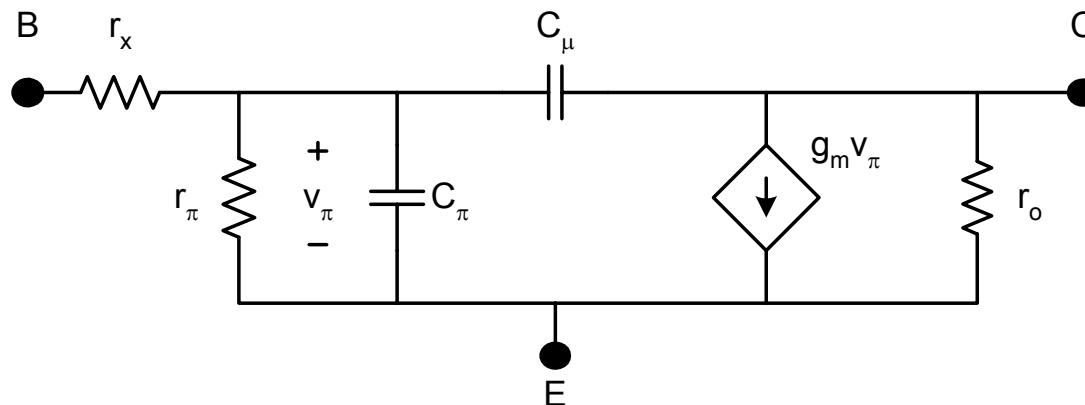
# High-Frequency Model of BJTs


- When we looked at pn junctions, we found that the depletion regions can be modeled as capacitances. Let's see how these capacitances affect the performance of BJTs.
- There are two depletion regions and therefore two capacitors we need to include into our small-signal model. Also, a base resistance  $r_x$  is added because of current crowding at high frequencies (second-order effect in BJTs).



- $C_\pi$  and  $C_\mu$  are bias dependent values which can be found (approximated) from the DC bias conditions of the circuit
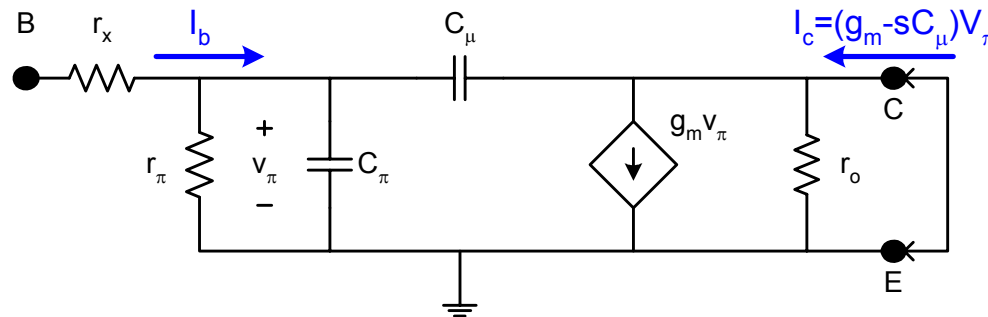
# $f_T$

- Transistor performance is often presented in terms of  $f_T$  which is a value that corresponds to its short-circuit current gain bandwidth product (or unity-gain bandwidth). Let's see how to solve for it...



- Find  $I_c/I_b$

$$V_\pi = I_b (r_\pi \parallel C_\pi \parallel C_\mu) \quad \frac{I_c}{I_b} = \frac{g_m - sC_\mu}{1/r_\pi + s(C_\pi + C_\mu)}$$

- at frequencies over which the model is valid,  $g_m \gg \omega C_\mu$

$$\frac{I_c}{I_b} \cong \frac{g_m r_\pi}{1 + s(C_\pi + C_\mu)r_\pi} = \frac{\beta_0}{1 + s(C_\pi + C_\mu)r_\pi}$$

$\beta_0$  is the low-frequency value of  $\beta$  and current gain rolls off with a single pole at  $\omega_\beta$

$$\omega_\beta = \frac{1}{(C_\pi + C_\mu)r_\pi} \quad \omega_T = \beta_0 \omega_\beta = \frac{g_m}{C_\pi + C_\mu} \rightarrow f_T = \frac{g_m / 2\pi}{C_\pi + C_\mu}$$